


Welcome to

Electric Machines & Drives

thomasblairpe.com/EMD



Thomas Blair, P.E.
USF Polytechnic – Engineering
tom@thomasblairpe.com

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Session 9:
Motor Control & Power Electronics

Fall 2011

Session 9

- Chapter 20 – Basics of Industrial Motor Control
- Chapter 21 – Fundamental Elements of Power Electronics (Part 1)

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20 – Basics of Industrial Motor Control

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)


Chapter 20


Starting, stopping, direction
Speed, Torque, Power – chapter 22/23
Size accordingly
Switches, breakers, Push Button, relays, contactors (starters), fuses, OL, Lights (annunciator), resistors, inductors, xfmsr, capacitors.
Symbols in Table 20A


USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC


Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)


Chapter 20

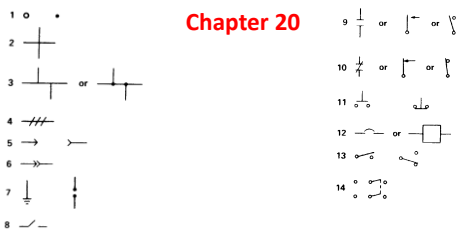


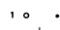
1 

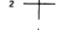
2 


3 

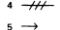
4 

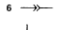
5 

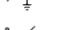
6 


7 


8 

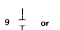
9 

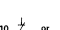10 

11 

12 

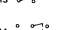
13 

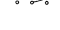
14 


USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC


Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)


Chapter 20

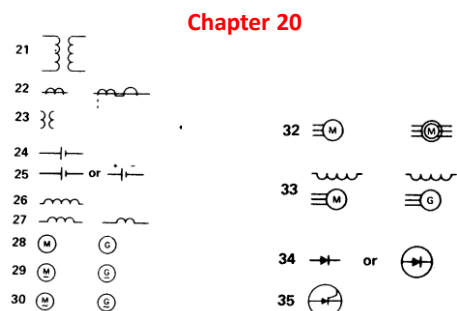

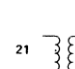

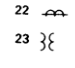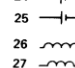21 


22 


23 

24 

25 

26 


27 


28 


29


30

31

32 

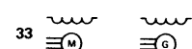33 

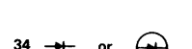34 

35 

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 20-1

A 3 phase NEMA size 5 magnetic contactor rated at 270A, 460V possesses a 120V, 60Hz relay coil. The coil absorbs an apparent power of 2970 VA and 212 VA, respectively, in the open and closed contactor position. Calculate

- The inrush exciting current
- The normal sealed exciting current
- The control power needed to actuate the relay coil

7



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

Control Diagrams –
Block Diagram – description of functions and interactions
One Line Diagram – More detail than block diagram –
Wiring Diagram – Detailed connection information in physical representation
Schematic diagram – Detailed connection information in logical sequence


8



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20


Block Diagram of Combination Starter

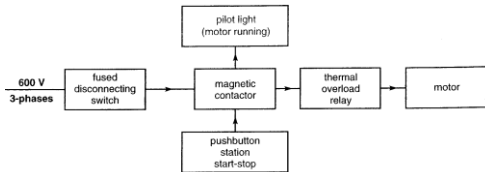

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20


One Line Diagram

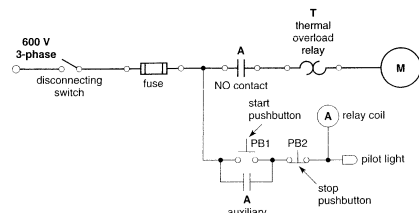

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20


Wiring Diagram

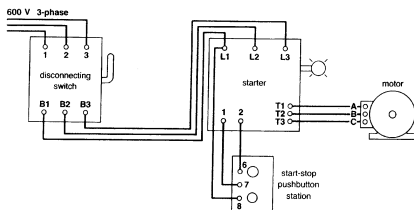

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20


Schematic Diagram

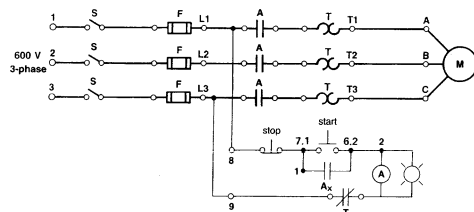

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

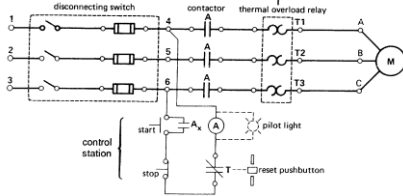ATL start – Simple, Large inrush, Large Torque
 Starter = Contactor + OL
 Combination starter = Starter + Switch (or CB)
 Purpose of OL vs Purpose of fuse?



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 20

Higher voltage starters – CPT – reduce control voltage
 Manual ATL starter vs Magnetic ATL starter?
 Simplicity
 Safety

14



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 20

OL curve –
 From cold condition
 Reduce about 30% if from hot condition
 Class 10 – @ 6X PU, trips in 10 sec from cold condition
 Class 20 – @ 6X PU, trips in 20 sec from cold condition
 Class 30 – @ 6X PU, trips in 30 sec from cold condition
 NEC requirements, conductor size, fuse size, etc


15



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 20


Overload Curve

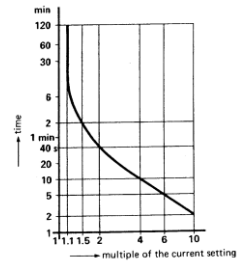

Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 20

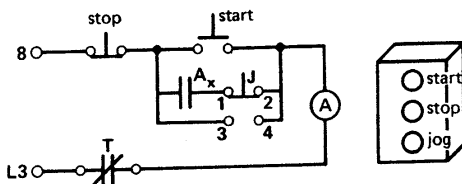
Inching / Jogging
 Severe contact duty –make/break currents
 Contactor oversized



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 20

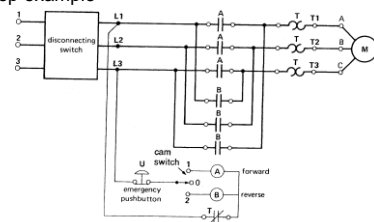
Reversing – change 2 lines
 Mechanical / electrical interlocks
 E-stop example



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 20


Plugging – Stop Motor

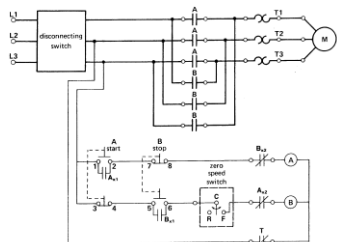

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

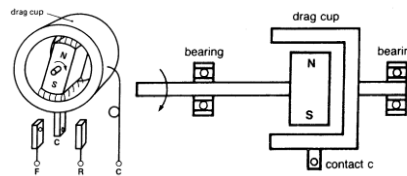
Zero Speed Switch –
PM drags cup in direction of rotation



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

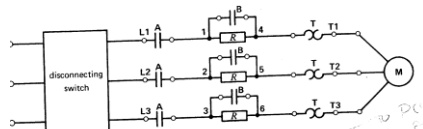
- Reduced Voltage Starting (softstart)
- Primary Resistance
- Primary Reactance
- Wye – Delta
- Auto Xfmr
- Partial winding start
- Solid state



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

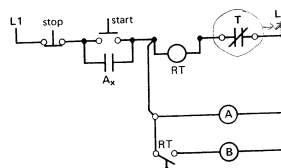
- Control circuit for primary resistance start
- T typically on common return
- Larger size contactors use circuit C for inrush
- Torque \propto voltage²



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

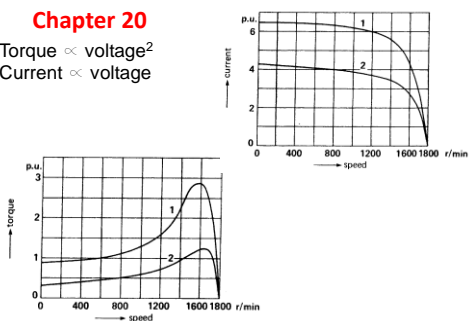- Torque \propto voltage²
- Current \propto voltage



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 20-2

A 150 kW (200HP), 460V, 3 phase, 3520 rpm, 60 Hz induction motor has a locked rotor torque of 600 Nm and a locked rotor current of 1400 A. Three resistor are connected in series with the line so as to reduce the voltage across the motor to 0.65 pu. Calculate

- a. The apparent power absorbed by the motor under full voltage, locked rotor conditions
- b. The apparent power absorbed y the motor when the resistors are in the circuit.
- c. The apparent power drawn from the line, with the resistor in the circuit
- d. The locked rotor torque developed by the motor

24



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 20-3

From Example 20-2, if the locked rotor power factor of the motor alone is 0.35, calculate the value of the series resistor and the power they dissipate.

25




Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Auto Transformer Starter Chapter 20

For given Torque – lower line current


Open transition
Closed transition

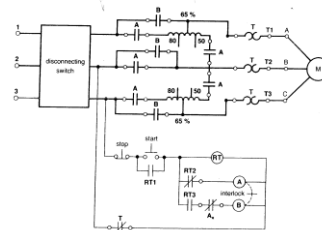

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

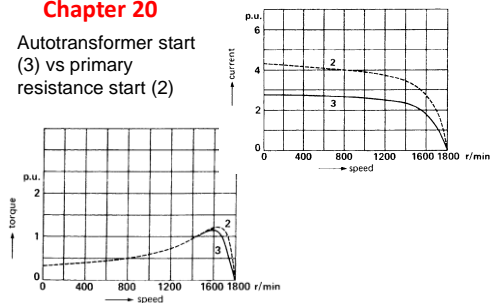Autotransformer start (3) vs primary resistance start (2)



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 20-4

A 200 HP (150 kW, 460V 3 phase, 3520 rpm, 60 Hz induction motor has a locked rotor torque of 600 Nm and a locked rotor current of 1400 A (Same motor as example 20-2). Two autotransformers connected in open delta and having a 65% tap, are employed to provide reduced voltage starting. Calculate

- The apparent power absorbed by the motor
- The apparent power supplied by the 460V line
- The current supplied by the 460V line
- The locked rotor torque


28



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

Part winding starter

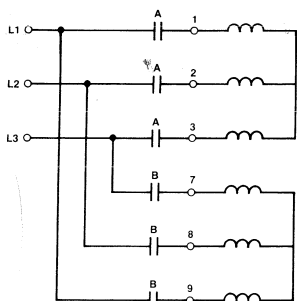

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

Wye delta starter
Start $V = V_{ll} / \sqrt{3}$

Torque = $T / 3$

SINGLE AND DUAL VOLTAGE WYE-DELTA CONNECTIONS



SINGLE VOLTAGE

OPERATING MODE	CONNECTION	L1	L2	L3	JOIN
START	WYE	1	2	3	4&5&6
RUN	DELTA	1,6	2,4	3,5	---



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

Drive Fundamentals – 4 quadrants of operation
More info in Chapters 20 - 22

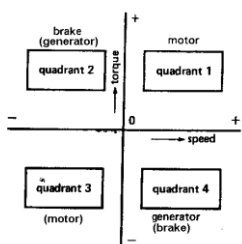


Figure 20.36
Electric drives can operate in four distinct quadrants. FIGURE MODIFIED FROM BOOK



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

Motor – Generator - Brake

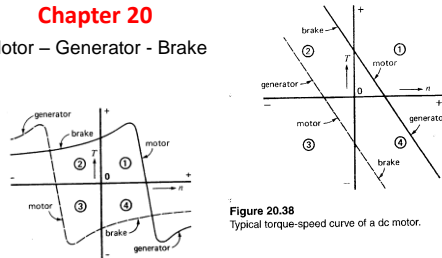


Figure 20.37
Typical torque-speed curve of a squirrel-cage induction motor operating at fixed voltage and frequency.

Figure 20.38
Typical torque-speed curve of a dc motor.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

Torque / speed curve AC induction machine

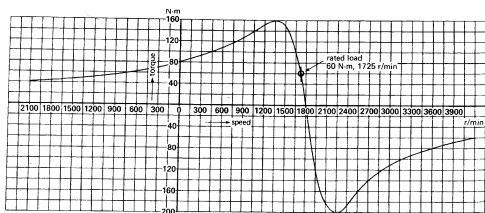


Figure 20.39
Torque-speed curve of a 15 hp, 480 V, 60 Hz, 3-phase, squirrel-cage induction motor.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

Varying Volts and Hertz on AC machines

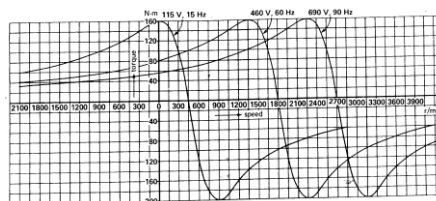


Figure 20.40
Torque-speed curve at three different frequencies and voltages.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

DC effect on Torque speed curve

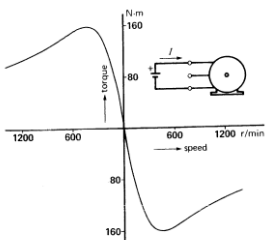


Figure 20.41
Stator excited by dc current.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Examble 20-5

A standard 3 phase, 10 HP, 575V, 1750 rpm, 60 Hz, NEMA class D squirrel cage induction motor develops a torque of 110 Nm at a speed of 1440 rpm. If the motor is excited at a frequency of 25 Hz, calculate the following:

- The required voltage to maintain the same flux in the machine
- The new speed at a torque of 110 Nm



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

Current vs Speed

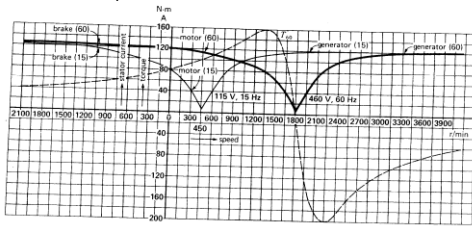


Figure 20.42
Current-speed curve at 60 Hz and 15 Hz. Also T-n curve at 460 V, 60 Hz



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 20-6

Using the information revealed by the 60Hz torque speed and current speed curves of figure 20.42, calculate the voltage and frequency required so that the machine will run at 3200 rpm while developing a torque of 100 Nm. What is the corresponding stator current?

38



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 20

If freq changed
F 60hz -> 30 hz
Motor speed still
1650RPM
1 - 2 - 3 - 4
Final motor speed
750
Note slip still 150 RPM
for same torque

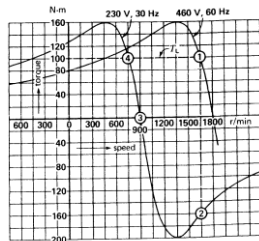


Figure 20.44
Effect of suddenly changing the stator frequency.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21 – Fundamental Elements of Power Electronics (Part 1)



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Power Electronics -> control of electric machine parameters such as Torque, Speed, Power.
Due to importance, deserves some study of subject for EMD.

41



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21, $V_{78} = 1/C \int i_c * dt$

$V_{56} = L * di/dt$

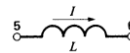


Figure 21.7
Potential across an inductor.



Figure 21.8
Potential across a capacitor.
Switch open - $V_{12} \neq 0$
Switch closed - $V_{12} = 0$

$V_{34} = I * R$

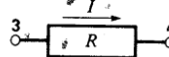


Figure 21.6
Potential across a resistor.

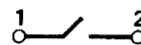



Figure 21.5
Potential across a switch.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

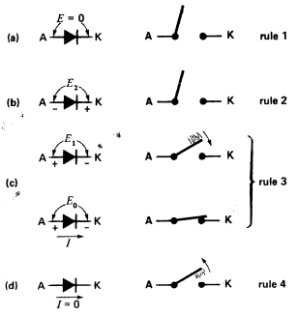
Diode Behavior
 $V_{ak} = 0 \rightarrow$ open
 $V_{ak} < 0 \rightarrow$ open
 $V_{ak} > 0 \rightarrow$ short
 $I > I_{hold} \rightarrow$ short
 $I < I_{hold} \rightarrow$ open
 PIV \rightarrow
 $I_{av(max)} \rightarrow$ max avg
 $T(max) \rightarrow$ max Temp
 Max di/dt (turnon)
 Max dv/dt (turnoff)



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

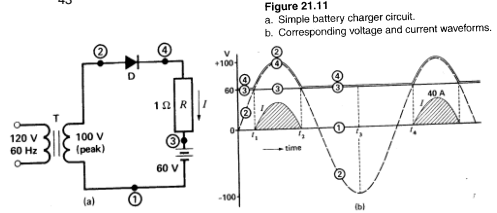
Resistive Battery Charger
 I^2R losses in resistor
 $I = E_{43}/R$



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

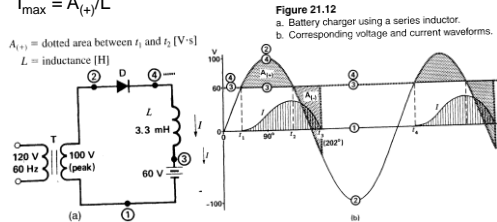
Inductive Battery Charger
 Stored Energy example
 $I_{max} = A_{(+)} / L$



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

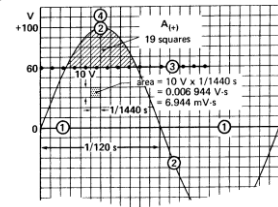Example 21-1

The coil below has an inductance of 3.3 mH and the battery voltage is 60V. Calculate the peak current if the line frequency is 60 Hz.



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

Single Phase Bridge Rectifier
 2 pulse rectifier
 Frippl = #pulse*fline
 = 2 * fline
 Ripple = 2*f(line)
 Ripple-p = Epeak

$E_d = 0.9 E$ $I_d = E_d/R = 0.9 E / R$
 E_d = dc voltage of single phase bridge rectifier (V)
 E = effective value of ac line voltage (V)

47



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

Single phase rectifier

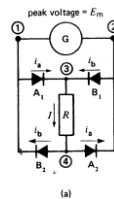


Figure 21.13
 a. Single-phase bridge rectifier.
 b. Voltage levels.

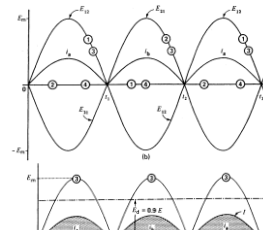


Figure 21.13c
 Voltage and current waveforms in load R.



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Example 21-2

The ac source in fig 21.13a has an effective voltage of 120V, 60Hz. The load draws a dc current of 20A. Calculate
 a. The dc voltage across the load
 b. The average dc current in each diode


49



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

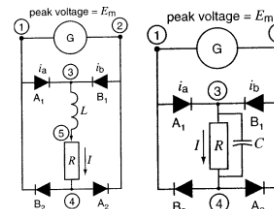
Filters –
 L – constant current
 Series w/ load
 Line current square wave
 C – constant voltage
 Parallel w/ load
 Line current spike
 a. Rectifier with inductive filter
 b. Rectifier with cap filter



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

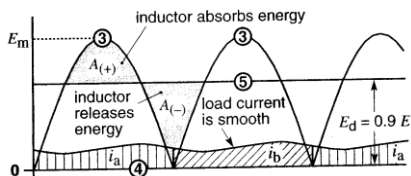L – constant current - Series
 C – constant voltage - Parallel
 Voltage and current waveforms in inductive filter



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

Ripple in single phase rectifier with filter

$$\text{Ripple} = (5.5 P) / (f WI)$$

Ripple = peak to peak current as % of dc current (%)
 WI = dc energy stored in the smoothing inductor (J)
 P = dc power drawn by the load (W)
 f = frequency of the source

52



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Example 21-3

We wish to build a 135V, 20A dc power supply using a single phase bridge rectifier and an inductive filter. The peak to peak current ripple should be about 10%. If a 60 Hz ac source is available, calculate the following;
 a. The effective value of the ac supply voltage
 b. The energy stored in the inductor
 c. The inductance of the inductor
 d. The peak to peak current ripple

53



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

3 phase, 3 pule rectifier

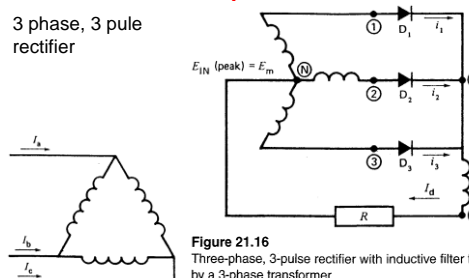


Figure 21.16
 Three-phase, 3-pulse rectifier with inductive filter fed by a 3-phase transformer.



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

3 pulses per cycle – Filter element L
 Conduction period $360^\circ / 3 \text{ pulses} = 120^\circ$ per pulse

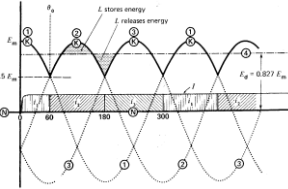


Figure 21.17
 Voltage and current waveforms in a 3-phase, 3-pulse rectifier.



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

Commutation – change of diode state from on to off

Natural or Line commutation – Line voltage forces commutation

Ripple voltage less than single phase

$$F_{\text{ripple}} = \# \text{pulse} * f_{\text{line}} = 3 * f_{\text{line}}$$

$$E_d = 0.675 E$$

E_d = average or dc voltage of a 3 pulse rectifier (V)

E = effective ac line voltage (V)

56



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

3 Phase, 6 pulse rectifier – $1.225 < E_d < 1.414$
 Peak to Peak $1.414 - 1.225 = 0.189 E$
 Frippl = Fline * Pulse #
 Frippl = Fline * 6

$$E_d = 1.35 E$$

E_d = dc voltage of 6 pulse rectifier (V)

E = effective line voltage (V)

57



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)


Chapter 21

3 phase, 6 pulse rectifier

$$I_a = i_1 - i_4$$

$$I_b = i_2 - i_5$$

$$I_c = i_3 - i_6$$

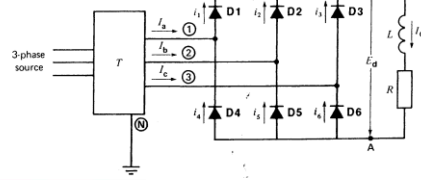

Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

Ripple - $PIV = E_{\text{peak}}$

Conduction $360^\circ / \# \text{pulse} = 360^\circ / 6 = 60^\circ$

$$\text{Ripple} = (0.17 P) / (f W I)$$

Ripple = peak to peak current as % of the dc current (%)

WI = dc energy stored in the inductor (J)

P = dc power drawn by the load (W)

f = frequency of the 3 phase, 6 pulse source)


59



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)


Chapter 21

Voltage and current waveforms

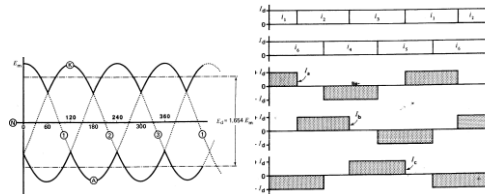


Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 21

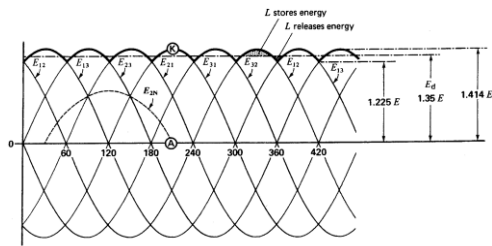

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

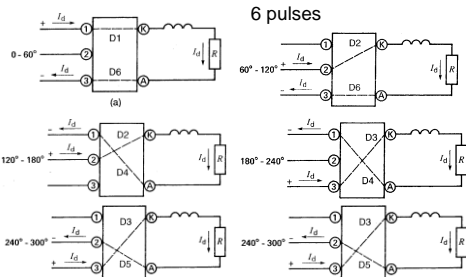

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 21-4

A 3 phase bridge rectifier has to supply power to a 360 kW, 240V dc load. If the 600V, 3 phase, 60 Hz feeder is available, calculate the following

- Voltage rating of the 3 phase transformer
- DC current per diode
- PIV across each diode
- Peak to peak ripple in the output voltage and its frequency



63
Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

- Calculate the inductance of the smoothing choke required in example 21-4 if the peak to peak ripple in the current is not to exceed 5%.
- Does the presence of the choke modify the peak to peak ripple in the output voltage E_{ka} ?



64
Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Relationship between I_d and I_{line}

$$I = \sqrt{(120/180)} I_d = 0.816 I_d$$

$$P_d = E_d I_d$$

$$P_{ac} = \sqrt{3} E I_f$$

$$I_f = 0.78 I_d = 0.955 I$$

I is effective value of line current
 I_f is fundamental value of line current



65
Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Total PF = PF Displacement & PF Distortion

PF = active power/apparent power

$$PF_{dist} = I_f/I \text{ but } I_f = 0.955 I$$

PF dist = 95.5% due to line current being rectangular



66
Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Total PF = PF Displacement & PF Distortion

Total PF = P / (E IL)

Displacement PF = P / (E If)

P = active power per phase (W)

E = effective value of voltage per phase (V)

IL = effective value of line current including fundamental and harmonics (A)

If = effective value of the fundamental component of line current (A)

67



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Harmonic Content and THD

N +/- 1

Amplitude = IF Amplitude / harmonic number

$$I_2 = I_f^2 + I_H^2$$

$$I_H^2 = I_{HA}^2 + I_{HB}^2 + I_{HC}^2 + I_{HD}^2 + \dots$$

$$THD = I_H / I_f$$

I = rms value of the line current

I_f = rms value of the fundamental component of line current

I_H = rms value of all the harmonic components combined.


68



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Harmonic Content and delay angle

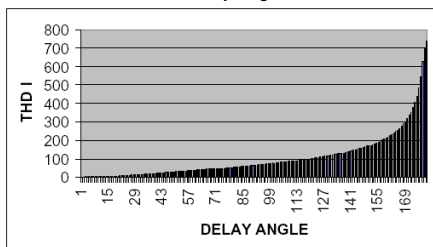

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 21-6

The 3 phase, 6 pulse rectifier in figure 21.19 furnishes a dc current of 400A to the load. Estimate, for line 1

- The effective value of the line current measured by an rms hook on ammeter
- The effective value of the fundamental component of line current
- The peak value of the 7th harmonic
- The rms value of the 7th and 11th harmonics combined.

70




Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Solid state switch – point of conduction controlled

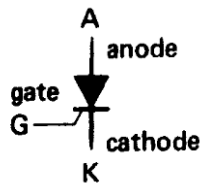- Anode positive
- Gate current injected
- Anode to cathode current remain positive



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)


Chapter 21

V_g = (+)

NPN pulling the N substrate low

PNP is gated


Current to flow from cathode to gate

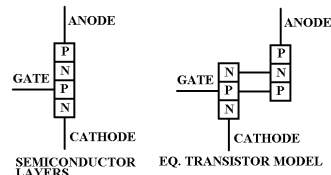

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Construction of "hockey puck"

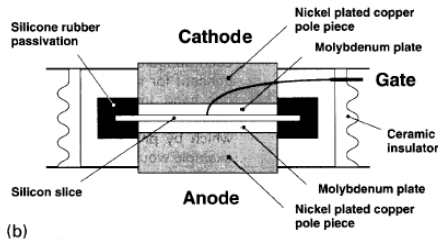

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Packaging:




USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Steady state model
Goal = Minimize T_j

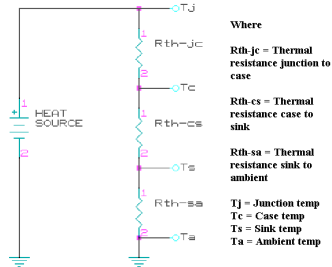

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

$T_j(\max) = 125^\circ\text{C}$
HS Thermostat = 90°C

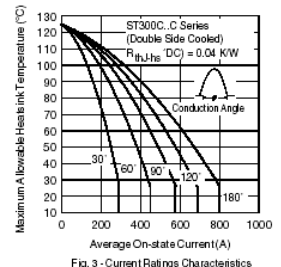


Fig. 3 - Current Ratings Characteristics

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

$P_{loss} = V_{ak} * I$
* # phases
Data sheet = P
* # devices

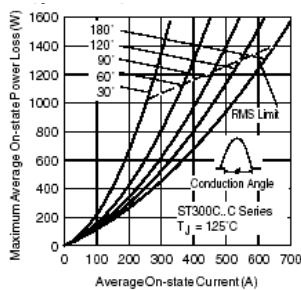



Fig. 5- On-state Power Loss Characteristics

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

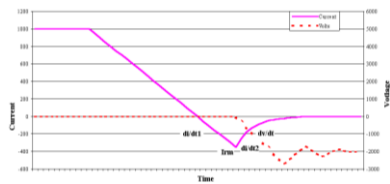SCR Critical Ratings:
PIV = Peak Inverse Voltage
RMS = Current rating (at T_j)
 di/dt = Rate of change of current
 Q_{rr} = Peak reverse recovery charge



USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Typical PIV ratings

Vrms	PIV
120	300
208	12:00 AM
240	600
380	1000
415	1000
440	1200
480	1200
575	1600
2300	6000
4160	12000
6600	18000
7200	18000
13800	36000


79



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

!!!SAFETY!!!
SCR output =
input voltage

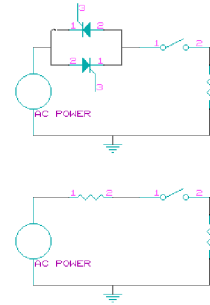

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Two Types of control

COMPARISON OF PHASE-ANGLE AND ZERO-CROSS		
PARAMETER	PHASE-ANGLE	ZERO-CROSS
Cost: 1-phase	Slightly more	Slightly less
Cost: 3-phase	Appreciably higher	2-leg control is appreciably less due to lower circuit cost and because only 2 of the 3 supply lines require SCR's. 3-leg control is slightly less because of circuit cost.
Type of loads:	Transformer coupled loads, fast responding loads, loads with large resistance changes, loads requiring current limiting, or soft start.	Resistive loads only. Power cannot be applied to a transformer. Moderately fast loads can be controlled with distributive control.
RFI and Harmonics (Ref Section 5)	Higher harmonics are generated and the potential for RFI is higher.	Harmonics and RFI are very low.
Reliability:	Lower than zero-cross	Higher than phase-angle because fewer components are required and because the SCR turns on when the voltage and current are zero.
Serviceability:	More complex	Easier because of fewer components.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21

Applications of control

ELEMENT TYPE	HOT / COLD RATIO	CONTROL TYPE
Molybdenum	15:0:1	Phase
Tungsten	20:1	Phase
Graphite	20:1	Phase
Nichrome	1.1:1	Zero
Tungsten	20:1	Phase
Iron Chromium	1.1:1	Zero
80/20 Nichrome	1.1:1	Zero
35/20 Nichrome	1.2:1	Zero
Silicon Carbide	0.8:1	Phase

82



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 21 next session



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Electric Machines & Drives

thomasblairpe.com/EMD



Thomas Blair, P.E.
USF Polytechnic - Engineering
tom@thomasblairpe.com



End of Session 9:
Motor Control &
Power Electronics

Spring 2011